## combinatorial function after orch. - process



CentraleSupélec

ICS M2 Degree - 2021-2022 - Advanced Digital Electronics

## Practical Session N°3 Realization of sequential operators

system clock

We want to create a clock divider, that is to say that starting from a clock at a frequency f we obtain Greg. / mbeger a clock at a frequency f/N, N being an integer defined in advance.

First, we will make a simple frequency divider with an even division factor = 2N.

We are going to create an entity called clock\_divider. The number N will be a generic parameter of the entity provided as an integer.

The clock divider will be achieved by means of a countdown counter from (N-1) to 0.

Each time the counter returns to 0, its output is inverted.? to do  $2\times$ 

For our application, this clock divider will be used in an Altera DE10-lite board which has a clock at 50 Mhz. We will choose N = 25,000,000 so as to obtain a clock at 1 Hz. This clock will be connected to one of the LEDs on the board in order to visualize the oscillation.

1°) Opening of the project

Sensitivity c. event modelling princ.


Ist b. trenslation as a process
c. counters

A in the TD3 subdirectory.

Company and variable

We are still working in BE\_ALTERA in the TD3 subdirectory.

 You launch quartus and you open the clock\_divider project. The project contains an already prepared clk div module containing the entity. You will write the architecture.



## 2°) Coding the clock divider

The divider will be described in a synchronous process controlled by the input clock and the reset signal.

The half division factor is defined by a generic parameter of the entity: factor

We will use 2 signals: 1 integer signal which serves as a counter (clkcnt), and a binary signal which codes the output (clkout).

The algorithm is as follows - defect resing edge

At each clock edge 🗢 -If clkent = 0 then

Clkcnt = factor-1

Clkout = not clkout

- creebe symbol files for eirrent pyp

else

Clkent = clkent-1

stide TOR

As in the previous BE, you write the code, you check it, then you build the project and you test on the board.  1 142 blink
3°) Code analysis: What is the logic instantiated by the line: "Clkent = clkent-1"  Same question for the line "Clkent = factor-1"  Substract feeteur by @ each alt count  4°) We now want to create a clock divider whose factor is programmable (it becomes an input for
4°) We now want to create a clock divider whose factor is programmable (it becomes an input for the entity) and we remove the parity condition from the division factor. The input factor becomes the actual division factor. In fact the effective division factor will be factor + 1.  The counter will now be encoded using an unsigned signal.
Copy the cld_div.vhd file to clk_div2.vhd
Integrate the new file into the project using the project -> add_remove file in project menu Edit the file in quartus by double_clicking on its name in the project navigator  Quartus Prime Lite Edition - C:/Users/benabe
Quartus Prime Lite Edition - C:/Users/benabe
File Edit View Project Assignments F
Quartus Prime Lite Edition - C:/Users/benabe  File Edit View Project Assignments F  SW[3.0]  1 H2  SW 0 7 1/2  Project Navigator Files  Value  Files  Value  To:/Frotrols2afron  SW3
Project Navigator Files
Files  Walue  Triffotiols2affon  SW2  SW3  Clk_divz.vhd  Frides  Triffotiols2affon  SW3  Frides  Triffotiols2affon  SW3
clk_divz.vhd
clk_div.vhd of a style = 3
clock_divider.bdf
Edit the file accordingly
- Change of the name of the entity - Factor becomes an input (we choose to encode it on 4 bits in order to have a division factor
ranging from 1 to 16 by shifting the value by one (2 is represented by 1, 16 is represented by 15))
- Clkcnt becomes a 4-bits unsigned type vector
- The algorithm becomes the following
If clkcnt = 0 then
Clkcnt = factor Clkout = 1
$\frac{1}{2}$ : $\frac{1}{2}$ collect = factor $\frac{1}{2}$ + 1 then
Clkout = 0
else 0111 7 -
Clkent = clkent-1
1117 16
Analyze the code: Processing -> Analyze current file  Create the symbol of the new divider File -> Create / Update -> create symbol for current file
Add the new divider after the previous one and connect its output to LEDR [1] Then compile the project download and test.
5°) Subsidiary question
Does the preceding code work if factor = $0$ ?
What would have to be done to make the divisor work even for this value:
cit-out c= cit-in when fockeur = "0000" else
cle-aut: